

EXPERIMENT 9 :-

COMBINATIONAL CIRCUITS

Page No. :

Date : | |

- A) AIM :- TO PERFORM THE ADDITION OF TWO BIT NUMBERS USING HALF ADDER.


TRUTH TABLE :-

INPUTS		OUTPUTS	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Boolean Exp. :-

$$\text{SUM}(S) = A \cdot \bar{B} + \bar{A} \cdot B$$

$$\text{CARRY}(C) = A \cdot B$$

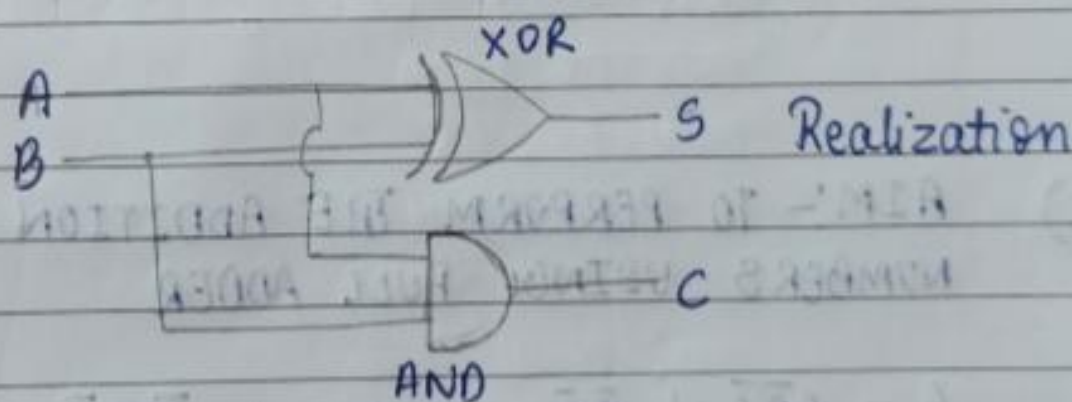

- B) AIM :- TO PERFORM THE SUBTRACTION OF TWO BIT NUMBERS USING HALF SUBTRACTOR


Boolean Expression :-

$$D = A'B + AB' = A \oplus B$$

$$B_0 = A'B$$

TRUTH TABLE:-

A	B	BORROW	DIFFERENCE
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

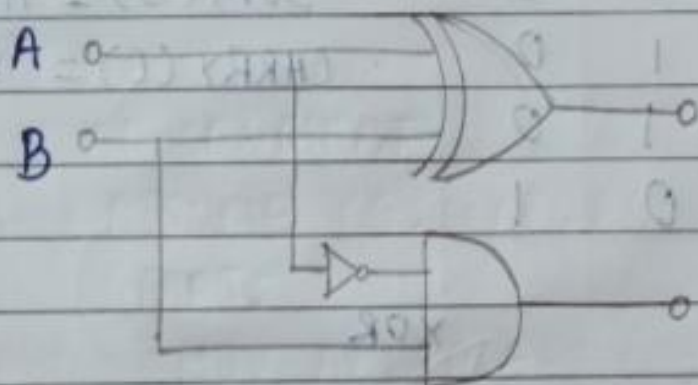

Realization

- c) AIM:- TO PERFORM THE ADDITION OF THREE BIT NUMBERS USING FULL ADDER

$$S = A\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}B\bar{C}$$

$$= C(\bar{A}B + A\bar{B}) + \bar{C}(\bar{A}B + A\bar{B})$$


$$= C(A \oplus B) + \bar{C}(A \oplus B) = A \oplus B \oplus C$$

$$C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= (A \oplus B) \cdot C + AB$$

TRUTH TABLE

INPUTS			OUTPUT	
A	B	Cin	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

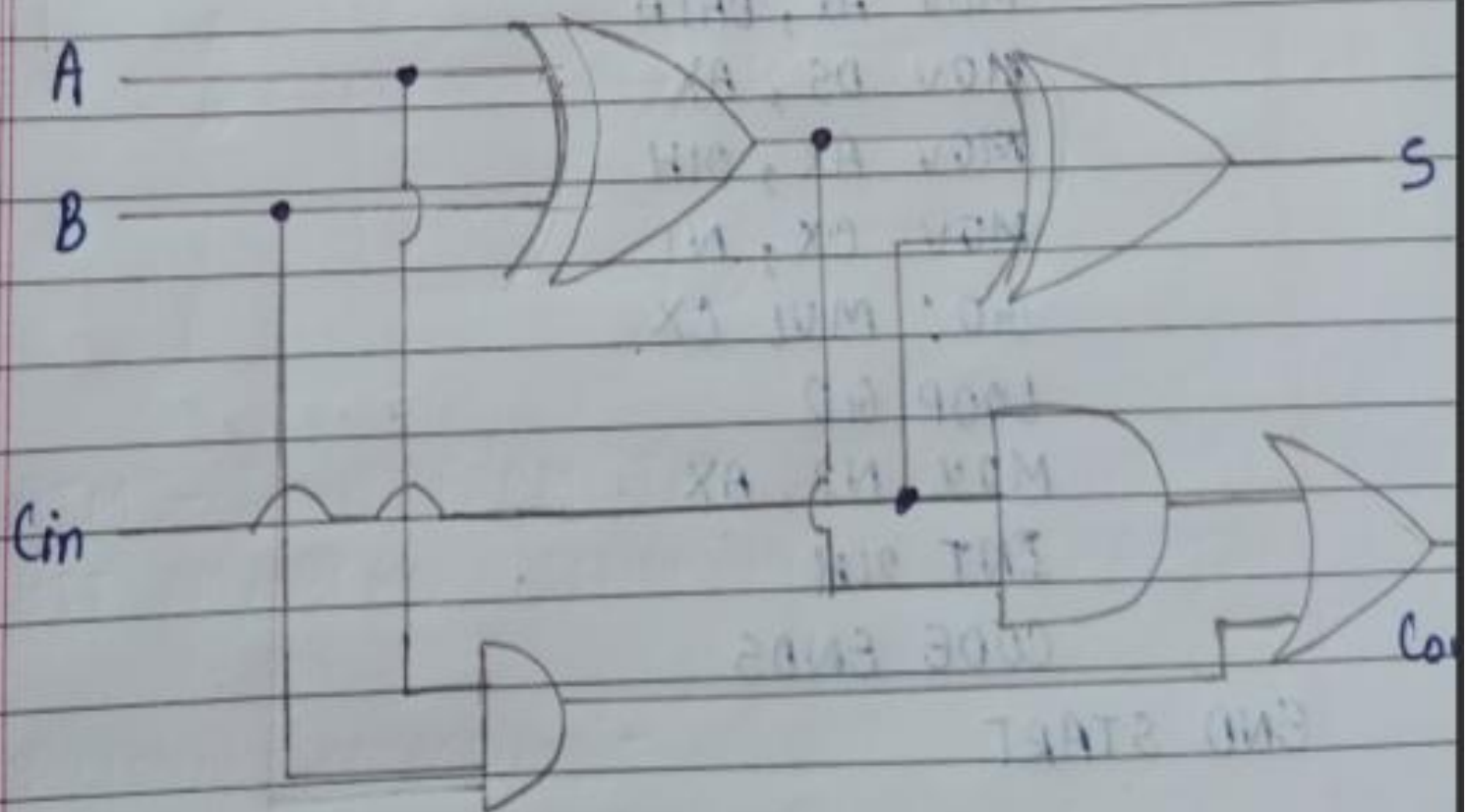

Full Adder


D) AIM:- TO FIND THE SUBTRACTION OF THREE BIT NUMBERS USING FULL SUBTRACTOR

$$\begin{aligned} D_1 &= A'(B'Bin + BBin') + A(B'Bin' + BBin) \\ &= A'(B \oplus Bin) + A(B \oplus Bin)' \\ &= A \oplus B \oplus Bin \end{aligned}$$

$$\begin{aligned} B_0 &= A'B'Bin + ABBin + A'B(Bin + Bin') \\ &= Bin(A \oplus B') + A'B \end{aligned}$$

TRUTH TABLE:-

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

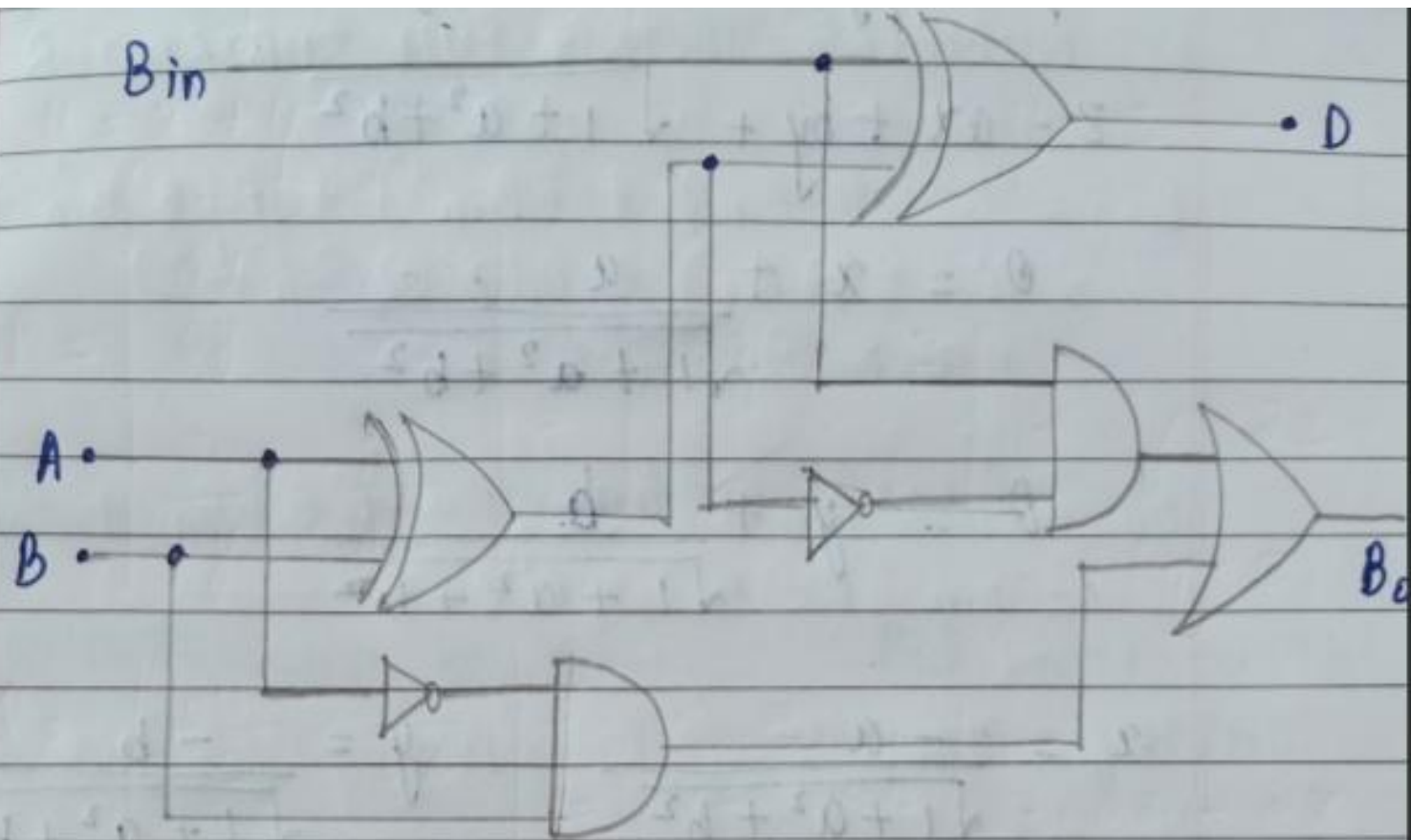

HALF SUBTRACTOR .

→ RESULT:-

The required operations are performed.